 


Пример “3-to-8 One-Hot” декодера (VHDL модел – конкурентна додела сигнала и логички оператори)



A	B	C	F7	F6	F5	F4	F3	F2	F1	F0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

$$F0 = \sum_{A,B,C}(0) = A'B'C'$$

$$F1 = \sum_{A,B,C}(1) = A'B'C$$

$$F2 = \sum_{A,B,C}(2) = A'B \cdot C'$$

$$F3 = \sum_{A,B,C}(3) = A'B \cdot C$$

$$F4 = \sum_{A,B,C}(4) = A \cdot B'C'$$

$$F5 = \sum_{A,B,C}(5) = A \cdot B'C$$

$$F6 = \sum_{A,B,C}(6) = A \cdot B \cdot C'$$

$$F7 = \sum_{A,B,C}(7) = A \cdot B \cdot C$$


```
entity decoder_1hot_3to8 is
  port (A,B,C          : in bit;
        F0,F1,F2,F3,F4,F5,F6,F7 : out bit);
end entity;

architecture decoder_1hot_3to8_arch of decoder_1hot_3to8 is
begin

  F0 <= (not A) and (not B) and (not C);
  F1 <= (not A) and (not B) and (C);
  F2 <= (not A) and (B)      and (not C);
  F3 <= (not A) and (B)      and (C);
  F4 <= (A)      and (not B) and (not C);
  F5 <= (A)      and (not B) and (C);
  F6 <= (A)      and (B)    and (not C);
  F7 <= (A)      and (B)    and (C);

end architecture;
```

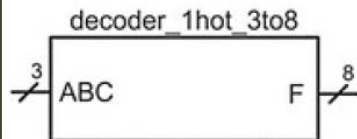Пример "3-to-8 One-Hot" декодера (VHDL модел – условна/селекциона додела сигнала)



ABC	F(7)	F(6)	F(5)	F(4)	F(3)	F(2)	F(1)	F(0)
"000"	0	0	0	0	0	0	0	1
"001"	0	0	0	0	0	0	1	0
"010"	0	0	0	0	0	1	0	0
"011"	0	0	0	0	1	0	0	0
"100"	0	0	0	1	0	0	0	0
"101"	0	0	1	0	0	0	0	0
"110"	0	1	0	0	0	0	0	0
"111"	1	0	0	0	0	0	0	0

```
entity decoder_1hot_3to8 is
  port (ABC : in bit_vector(2 downto 0);
        F : out bit_vector(7 downto 0));
end entity;
```

```
architecture decoder_1hot_3to8_arch of decoder_1hot_3to8 is
begin
  F <= "00000001" when (ABC = "000") else
       "00000010" when (ABC = "001") else
       "00000100" when (ABC = "010") else
       "00001000" when (ABC = "011") else
       "00010000" when (ABC = "100") else
       "00100000" when (ABC = "101") else
       "01000000" when (ABC = "110") else
       "10000000" when (ABC = "111");
end architecture;
```

```
architecture decoder_1hot_3to8_arch of decoder_1hot_3to8 is
begin
  with (ABC) select
    F <= "00000001" when "000",
         "00000010" when "001",
         "00000100" when "010",
         "00001000" when "011",
         "00010000" when "100",
         "00100000" when "101",
         "01000000" when "110",
         "10000000" when "111";
end architecture;
```

Декодер за 7-сегментни дисплеј (VHDL модел – конкурентна додела сигнала и логички оператори)

decoder_7seg			A	B	C	Fa	Fb	Fc	Fd	Fe	Ff	Fg
— A — B — C	Fa Fb Fc Fd Fe Ff Fg	— — — — — — —	0	0	0	1	1	1	1	1	1	0
			0	0	1	0	1	1	0	0	0	0
			0	1	0	1	1	0	1	1	0	1
			0	1	1	1	1	1	1	0	0	1
			1	0	0	0	1	1	0	0	1	1
			1	0	1	1	0	1	1	0	1	1
			1	1	0	1	0	1	1	1	1	1
			1	1	1	1	1	1	0	0	0	0

```


entity decoder_7seg is
    port (A,B,C          : in bit;
          Fa,Fb,Fc,Fd,Fe,Fg,Fg : out bit);
end entity;

architecture decoder_7seg_arch of decoder_7seg is
begin
    Fa <= ((not A) and (not C)) or B or (A and C);
    Fb <= ((not B) and (not C)) or (not A) or (B and C);
    Fc <= A or (not B) or C;
    Fd <= ((not A) and (not C)) or ((not A) and B) or (B and (not C))
        or (A and (not B) and C);
    Fe <= ((not A) and (not C)) or (B and (not C));
    Ff <= ((not B) and (not C)) or (A and (not C)) or (A and (not B));
    Fg <= ((not A) and B) or (A and (not C)) or (A and (not B));

end architecture;

```

 Декодер за 7-сегментни дисплеј (VHDL модел – условна/селекциона додела сигнала)



ABC	a F(6)	b F(5)	c F(4)	d F(3)	e F(2)	f F(1)	g F(0)
"000"	1	1	1	1	1	1	0
"001"	0	1	1	0	0	0	0
"010"	1	1	0	1	1	0	1
"011"	1	1	1	1	0	0	1
"100"	0	1	1	0	0	1	1
"101"	1	0	1	1	0	1	1
"110"	1	0	1	1	1	1	1
"111"	1	1	1	0	0	0	0

```

entity decoder_7seg is
  port (ABC : in bit_vector(2 downto 0);
        F   : out bit_vector(6 downto 0));
end entity;
  
```


```

architecture decoder_7seg_arch of decoder_7seg is
begin
  F <= "1111110" when (ABC = "000") else
        "0110000" when (ABC = "001") else
        "1101101" when (ABC = "010") else
        "1111001" when (ABC = "011") else
        "0110011" when (ABC = "100") else
        "1011011" when (ABC = "101") else
        "1011111" when (ABC = "110") else
        "1110000" when (ABC = "111");
end architecture;
  
```

```

architecture decoder_7seg_arch of decoder_7seg is
begin
  with (ABC) select
    F <= "1111110" when "000",
        "0110000" when "001",
        "1101101" when "010",
        "1111001" when "011",
        "0110011" when "100",
        "1011011" when "101",
        "1011111" when "110",
        "1110000" when "111";
end architecture;
  
```

 Пример “4-to-2 One-Hot” кодера (VHDL модел – конкурентна/условна/селекциона додела сигнала)



ABCD	YZ
"0001"	"00"
"0010"	"01"
"0100"	"10"
"1000"	"11"


```
entity encoder_1hot_4to2 is
    port (ABCD : in bit_vector(3 downto 0);
          YZ   : out bit_vector(1 downto 0));
end entity;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    YZ(1) <= ABCD(3) or ABCD(2);
    YZ(0) <= ABCD(3) or ABCD(1);
end architecture;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    YZ <= "00" when (ABCD = "0001") else
          "01" when (ABCD = "0010") else
          "10" when (ABCD = "0100") else
          "11" when (ABCD = "1000") else
          "00";
end architecture;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    with (ABCD) select
        YZ <= "00" when "0001",
              "01" when "0010",
              "10" when "0100",
              "11" when "1000",
              "00" when others;
end architecture;
```

 Пример “4-to-2 One-Hot” кодера (VHDL модел – конкурентна/условна/селекциона додела сигнала)



ABCD	YZ
"0001"	"00"
"0010"	"01"
"0100"	"10"
"1000"	"11"


```
entity encoder_1hot_4to2 is
    port (ABCD : in bit_vector(3 downto 0);
          YZ   : out bit_vector(1 downto 0));
end entity;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    YZ(1) <= ABCD(3) or ABCD(2);
    YZ(0) <= ABCD(3) or ABCD(1);
end architecture;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    YZ <= "00" when (ABCD = "0001") else
          "01" when (ABCD = "0010") else
          "10" when (ABCD = "0100") else
          "11" when (ABCD = "1000") else
          "00";
end architecture;
```

```
architecture encoder_1hot_4to2_arch of encoder_1hot_4to2 is
begin
    with (ABCD) select
        YZ <= "00" when "0001",
              "01" when "0010",
              "10" when "0100",
              "11" when "1000",
              "00" when others;
end architecture;
```

 
Пример “2-to-1 мултиплексера (VHDL модел – конкурентна/условна/селекциона додела сигнала)



Sel	F
"00"	A
"01"	B
"10"	C
"11"	D


```
entity mux_4to1 is
  port (A,B,C,D : in bit;
        Sel      : in bit_vector(1 downto 0);
        F        : out bit);
end entity;
```

```
architecture mux_4to1_arch of mux_4to1 is
begin
  F <= (A and not Sel(0) and not Sel(1)) or
       (B and not Sel(0) and      Sel(1)) or
       (C and      Sel(0) and not Sel(1)) or
       (D and      Sel(0) and      Sel(1));
end architecture;
```

```
architecture mux_4to1_arch of mux_4to1 is
begin
  F <= A when (Sel = "00") else
       B when (Sel = "01") else
       C when (Sel = "10") else
       D when (Sel = "11");
end architecture;
```

```
architecture mux_4to1_arch of mux_4to1 is
begin
  with (Sel) select
    F <= A when "00",
         B when "01",
         C when "10",
         D when "11";
end architecture;
```

 Пример “1-to-2 демултиплексера (VHDL модел – конкурентна/условна/селекциона додела сигнала)



Sel	W	X	Y	Z
"00"	A	0	0	0
"01"	0	A	0	0
"10"	0	0	A	0
"11"	0	0	0	A

```
entity demux_1to4 is
  port (A      : in  bit;
        Sel    : in  bit_vector(1 downto 0);
        W,X,Y,Z : out bit);
end entity;
```

```
architecture demux_1to4_arch of demux_1to4 is
begin
  W <= A and not Sel(0) and not Sel(1);
  X <= A and not Sel(0) and      Sel(1);
  Y <= A and      Sel(0) and not Sel(1);
  Z <= A and      Sel(0) and      Sel(1);
end architecture;
```

```
architecture demux_1to4_arch of demux_1to4 is
begin
  W <= A when (Sel = "00") else '0';
  X <= A when (Sel = "01") else '0';
  Y <= A when (Sel = "10") else '0';
  Z <= A when (Sel = "11") else '0';
end architecture;
```

```
architecture demux_1to4_arch of demux_1to4 is
begin
  with (Sel) select
    W <= A when "00", '0' when others;

  with (Sel) select
    X <= A when "01", '0' when others;

  with (Sel) select
    Y <= A when "10", '0' when others;

  with (Sel) select
    Z <= A when "11", '0' when others;
end architecture;
```